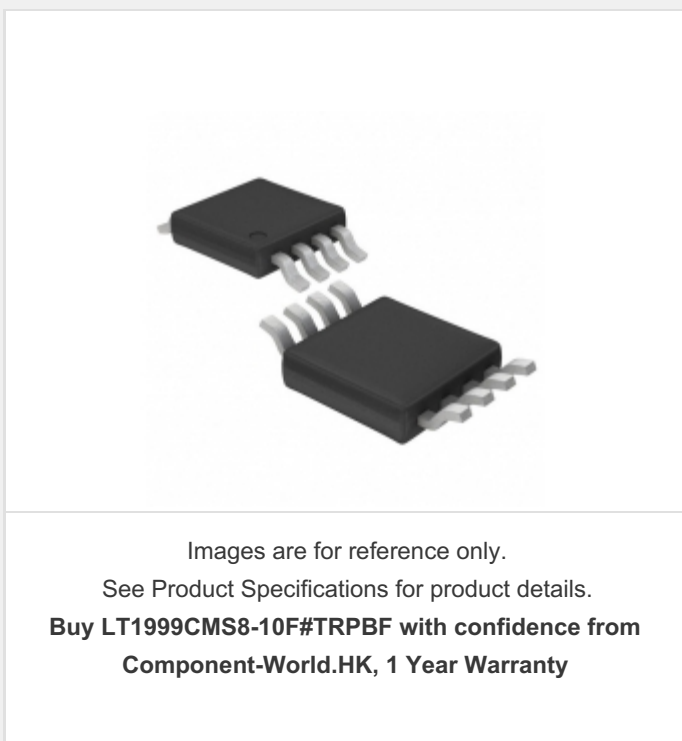


LT1999CMS8-10F#TRPBF



Part Number: [LT1999CMS8-10F#TRPBF](#)
Manufacturer: [ADI \(Analog Devices, Inc.\)](#)
Description: IC OP AMP CUR SENSE 2MHZ 8MSOP
Data sheet: [LT1999-10,20,50 Datasheet](#)
[Mac OS X Shortcuts](#)
[LTspice Flyer](#)
[LTspice IV Getting Started Guide](#)

RoHS Status: Lead free / RoHS Compliant
Ship From: Hong Kong
Shipment Way: DHL/Fedex/TNT/UPS/EMS

[Request For Quotation](#)

PRODUCT PARAMETER			
Part Number	LT1999CMS8-10F#TRPBF	Manufacturer	ADI (Analog Devices, Inc.)
Description	IC OP AMP CUR SENSE 2MHZ 8MSOP	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Quantity Available	45899 pcs	Data sheet	LT1999-10,20,50 Datasheet Mac OS X Shortcuts LTspice Flyer LTspice IV Getting Started Guide
Category	Integrated Circuits (ICs)	Voltage - Supply, Single/Dual (±)	4.5 V ~ 5.5 V
Voltage - Input Offset	500µV	Supplier Device Package	8-MSOP
Slew Rate	3 V/µs	Series	-
Packaging	Tube	Package / Case	8-TSSOP, 8-MSOP (0.118", 3.00mm Width)
Output Type	-	Operating Temperature	0°C ~ 70°C
Number of Circuits	1	Mounting Type	Surface Mount
Moisture Sensitivity Level (MSL)	1 (Unlimited)	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Detailed Description	Current Sense Amplifier 1 Circuit 8-MSOP	Current - Supply	5.8mA
Current - Output / Channel	40mA	Current - Input Bias	137.5µA
Base Part Number	LT1999	Amplifier Type	Current Sense
-3db Bandwidth	2MHz		

Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all ADI (Analog Devices, Inc.) series electronic components. We have 45899 pieces of ADI (Analog Devices, Inc.) LT1999CMS8-10F#TRPBF in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours.

RFQ Email: info@Components-World.com

RELATED PRODUCTS

	Part#: LT1997IDF-2#TRPBF Description: PRECISION, WIDE VOLTAGE RANGE, D	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-20F#TRPBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-50#PBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-20#TRPBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1997IDF-3#TRPBF Description: IC OP AMP RR 1.1MHZ 14DFN	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-50#TRPBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-20F#PBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-20#PBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CS8-10#PBF Description: IC OPAMP CURRENT SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1997IMS-2#PBF Description: PRECISION, WIDE VOLTAGE RANGE, D	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CS8-10#TRPBF Description: IC OPAMP CURRENT SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-10F#PBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1997IMS-3#TRPBF Description: IC OP AMP RR 1.1MHZ 16MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1997IMS-2#TRPBF Description: PRECISION, WIDE VOLTAGE RANGE, D	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1997IDF-3#PBF Description: IC OPAMP DIFF WIDE VOLTAGE RANGE	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-10#PBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-10#TRPBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1997IMS-3#PBF Description: IC OP AMP RR 1.1MHZ 16MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-50F#PBF Description: IC OP AMP CUR SENSE 1.2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999CMS8-50F#TRPBF Description: IC OP AMP CUR SENSE 1.2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ

Related keywords for **LT1999CMS8-10F#TRPBF**

ADI (Analog Devices, Inc.) LT1999CMS8-10F#TRPBF	LT1999CMS8-10F#TRPBF distributor	LT1999CMS8-10F#TRPBF supplier	LT1999CMS8-10F#TRPBF price
	LT1999CMS8-10F#TRPBF download datasheet	LT1999CMS8-10F#TRPBF datasheet	LT1999CMS8-10F#TRPBF stock
buy LT1999CMS8-10F#TRPBF	ADI (Analog Devices, Inc.) LT1999CMS8-10F#TRPBF	AD LT1999CMS8-10F#TRPBF	ADI (Analog Devices, Inc.) LT1999CMS8-10F#TRPBF
Analog Devices Inc. LT1999CMS8-10F#TRPBF	Analog Devices, Inc. LT1999CMS8-10F#TRPBF		